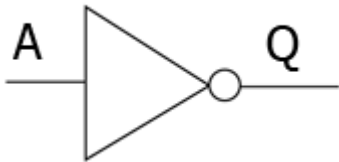


Logic Gates and Circuits

Question 1


The diagram below is for a NOT gate (or an Inverter) . Complete the truth table for this gate.



Input	Output
A	Q

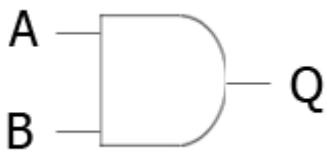Question 2


The diagram below is for an AND gate. Complete the truth table for this gate



Inputs		Output
A	B	Q

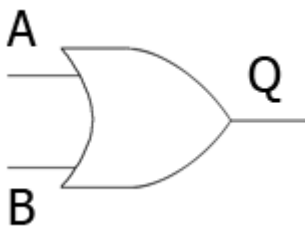Question 3

The diagram below is for an OR gate. Complete the truth table for this gate.



Inputs		Output
A	B	Q

Logic Circuits – A Combination of Logic Gates

Question 4

Complete this table to show every possible combination of logic 2 inputs for A and B


A	B

Question 5

Complete this table to show every possible combination of logic 3 inputs A, B and C

A	B	C

Question 6.

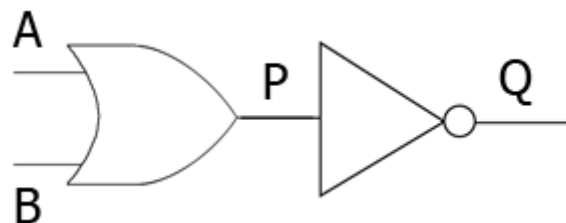


a) Complete the truth table for point P

Inputs		Outputs	
A	B	P	Q

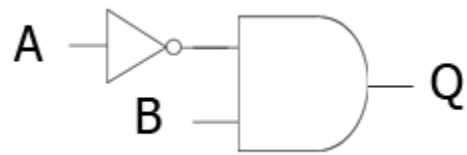Question 7


Complete the truth table for this circuit.



Inputs		Outputs	
A	B		

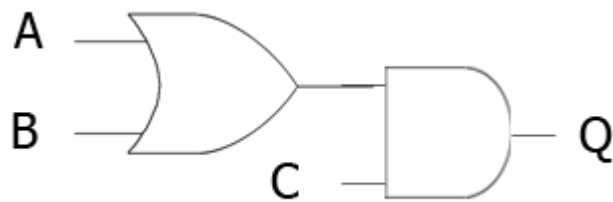Question 8

The logic circuit below has 3 inputs and so there are 8 possible combinations of A, B and C.




Now work out every value of Q for the circuit

Inputs			Outputs	
A	B	C	A OR B	Q

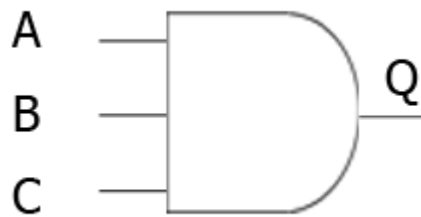Question 9

You can have more than two inputs to a logic gate.



Using the diagram above, complete the truth table below for the three input AND gate.

Inputs			Output
A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	